

Task 1 exp05 Data Tables

Fill up the table for the Flash AD Converter.

Input Voltage V_{IN} $=V_A$	State of LED1	State of LED0	Digital Binary Output
0.00	ON	ON	00
0.644	ON	OFF	01
1.84	OFF	ON	10
3.15	OFF	OFF	11

Table 1: Data Table for Flash AD Converter